

CSE332 Lab 5

Name: Nazmul Hasan

ID: 1911742042

Course: CSE332L

Section: 3

Experiment Name: Design of a 3-bit Binary Up-Down counter.

Table:

M	A	B	C	Q _A	Q _B	Q _C	T _A	T _B	T _C
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	1	0	0	0	1

By using 4 variable K-map, we can find the equation for T_A, T_B, and T_C.

K-map for T_A :

T_A	$B'C'$	$B'C$	BC	BC'
$M'A'$	0	0	1	0
$M'A$	0	0	1	0
MA	1	0	0	0
MA'	1	0	0	0

$$T_A = MB'C' + M'BC$$

K-map for T_B :

T_B	$B'C'$	$B'C$	BC	BC'
$M'A'$	0	1	1	0
$M'A$	0	1	1	0
MA	1	0	0	1
MA'	1	0	0	1

$$T_B = M'C + MC'$$

K-map for T_C :

T_C	$B'C'$	$B'C$	BC	BC'
$M'A'$	1	1	1	1
$M'A$	1	1	1	1
MA	1	1	1	1
MA'	1	1	1	1

$$T_C = 1$$

Discussion: In this lab our objective was to design a 4-bit a binary up-down counter. In our lab class, we implemented a 3-bit binary up down counter with a mode control. A counter that follows the binary number sequence is called a binary counter. We have used 'M' as mode control bit. When M is low (M=0), the counter counts downward and, when M is high (M=1), the counter counts upward. Variables A, B and C are used to represent states from 0 to 7. For each state, there is a next state. Q_A , Q_B and Q_C represent next states.

To design the up-down counter we have used T flip flops. The T flip flops act as a toggle switch. When the input is 0, there is no change in the output of the T flip-flops. It retains the previous value. But when the input is 1, the output is complemented. A XOR gate combined with a D flip-flop is used to create a T flip-flop.

A circuit excitation table is created where,

$$T_A = A \text{ XOR } Q_A, \quad T_B = B \text{ XOR } Q_B \text{ and } T_C = C \text{ XOR } Q_C$$

After that, we have used K-map to find the input equations for T_A , T_B and T_C . The input equations are:

$$T_A = MB'C' + M'BC, \quad T_B = M'C + MC' \text{ and } T_C = 1$$

With this input equations for three T flip flops we can create our 3-bit binary up down counter. From each flip flop output we will get three output bits Q_A , Q_B and Q_C that represent the next states.