



Lab Manual

Department of Electrical and Computer Engineering

School of Engineering and Physical Sciences

North South University, Bashundhara, Dhaka-1229, Bangladesh

Experiment No: 2

Experiment Name: Design of a 4-bit Arithmetic unit.

Introduction:

In this experiment you will construct a 4-bit arithmetic unit which is a part of an ALU. The arithmetic unit will be used to add and subtract two variables 4-bit inputs, A and B, as well as increment, decrement or transfer any of the inputs.

Arithmetic Operations:

Add- Each bit of input A is added with the corresponding bit of input B and the sum appears at the output of each full adder along with any carry out.

Add with carry- Each bit of input A and B are added with the input carry and the sum appears at the output of each full adder along with any carry out.

Subtract- Each bit of input B is subtracted from the corresponding bit of input A and the difference appears at the output of each full adder along with any borrow out.

Subtract with borrow- Each bit of input B is subtracted from A with borrow. The difference and the borrow out appear at the output.

Increment A- Each bit of A is increased by 1 and the result appears at the output of each full adder.

Decrement A- Each bit of A is decreased by 1 and the result appears at the output of each full adder.

Transfer A- Each bit of A appears at the output of each full adder, unmodified.

Select			Input Y	Output $D = A + Y + C_{in}$	Microoperation
S_1	S_0	C_{in}			
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	\overline{B}	$D = A + \overline{B}$	Subtract with borrow
0	1	1	\overline{B}	$D = A + \overline{B} + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

Equipment List:

- Trainer board
- IC 7404, 7483 or 74283, 74LS153
- Wires for connection.

Function Table:

Complete the function table according to your theoretical knowledge.

S1	S0	Cin	A3	A2	A1	A0	B3	B2	B1	B0	Cout	D3	D2	D1	D0	Microoperation
0	0	0	0	0	0	1	0	0	0	1						Add
0	0	1	0	0	1	1	0	1	0	0						Add with Carry
0	1	0	0	0	1	0	1	1	0	0						Subtract with Borrow
0	1	1	0	1	1	1	0	1	0	0						Subtract
1	0	0	1	0	1	1	0	1	0	0						Transfer A
1	0	1	0	1	0	0	0	0	0	0						Increment A
1	1	0	1	0	1	0	1	0	0	0						Decrement A
1	1	1	1	0	0	1	0	1	1	1						Transfer A

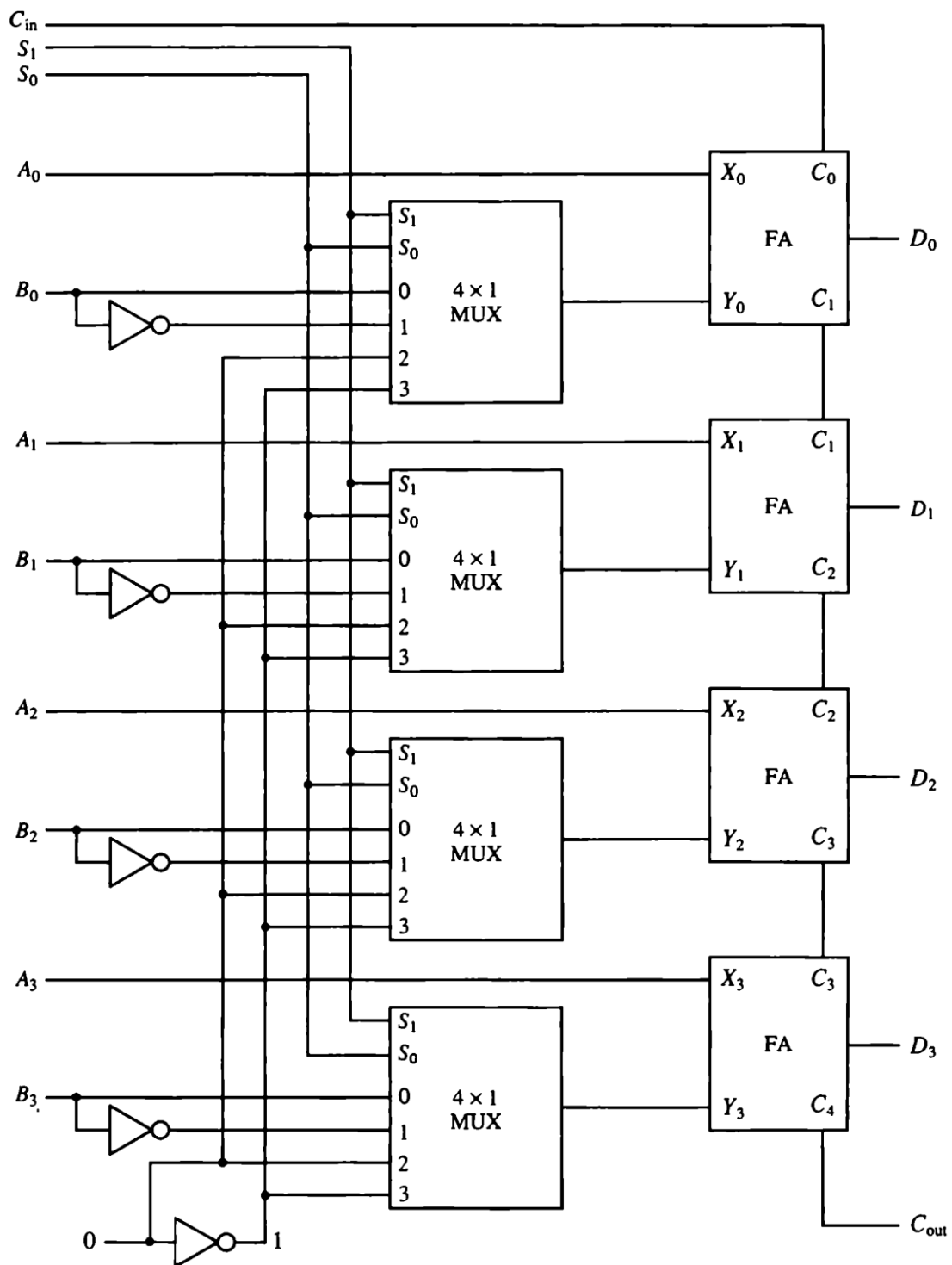
Logic Circuit Diagram:




Fig: 4-bit Arithmetic unit Logic Circuit Diagram

Procedure:

- 1) Place the ICs on the trainer board.
- 2) Connect V_{cc} and ground to the respective pins of IC.
- 3) Connect the inputs with the switches and the outputs with LEDs.
- 4) Apply various combinations of inputs and observe the outputs.
- 5) Verify the experimental outputs with the Function Table.

Assignment:

- 1) Prepare the lab report.
- 2) Implement the circuit in Logisim. Take a screenshot along with table in Logisim and include it in your lab report.

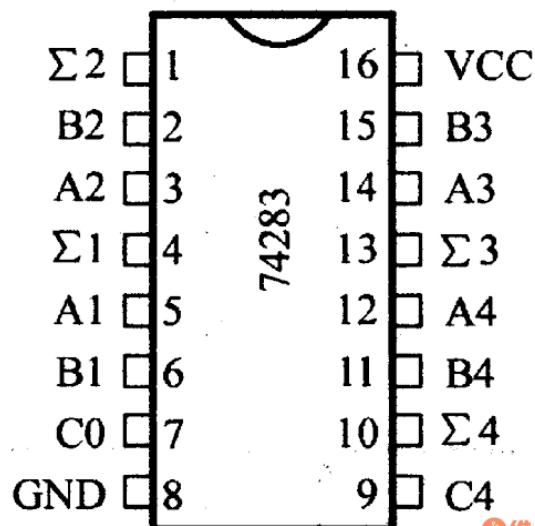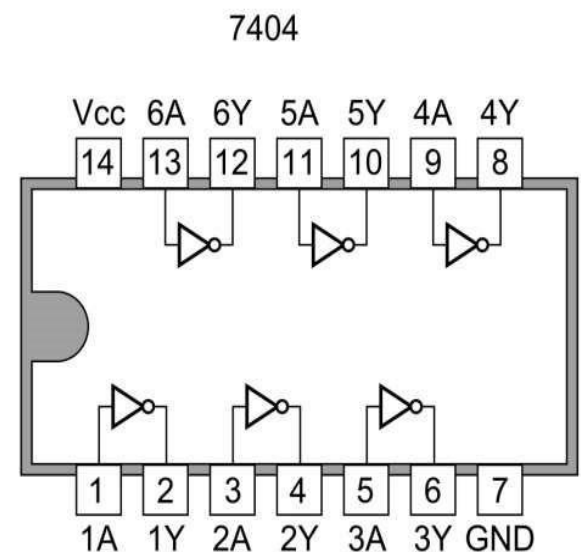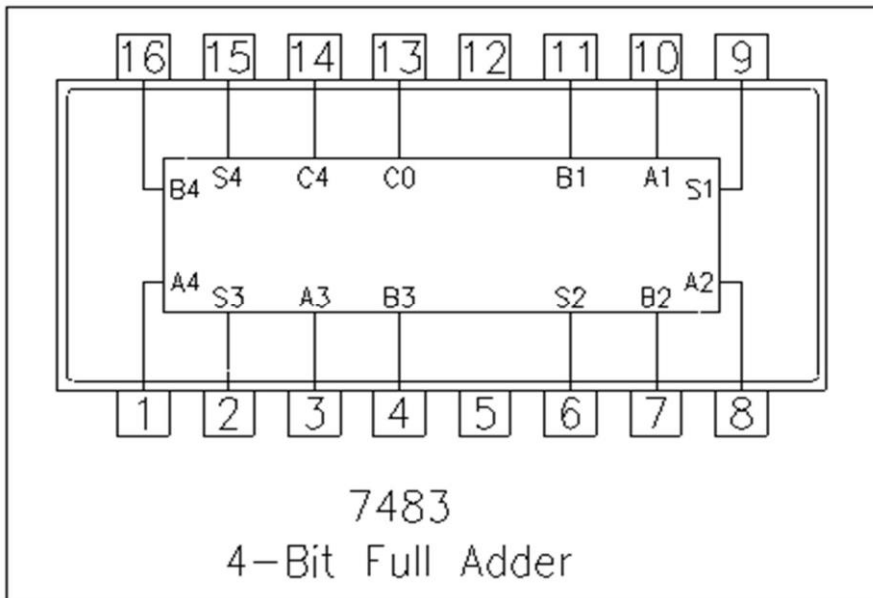
Pin configuration of ICs:

EEE336/CSE232 LAB

Dual 4x1 Multiplexer 74F153

Data Sheet

PIN CONFIGURATION

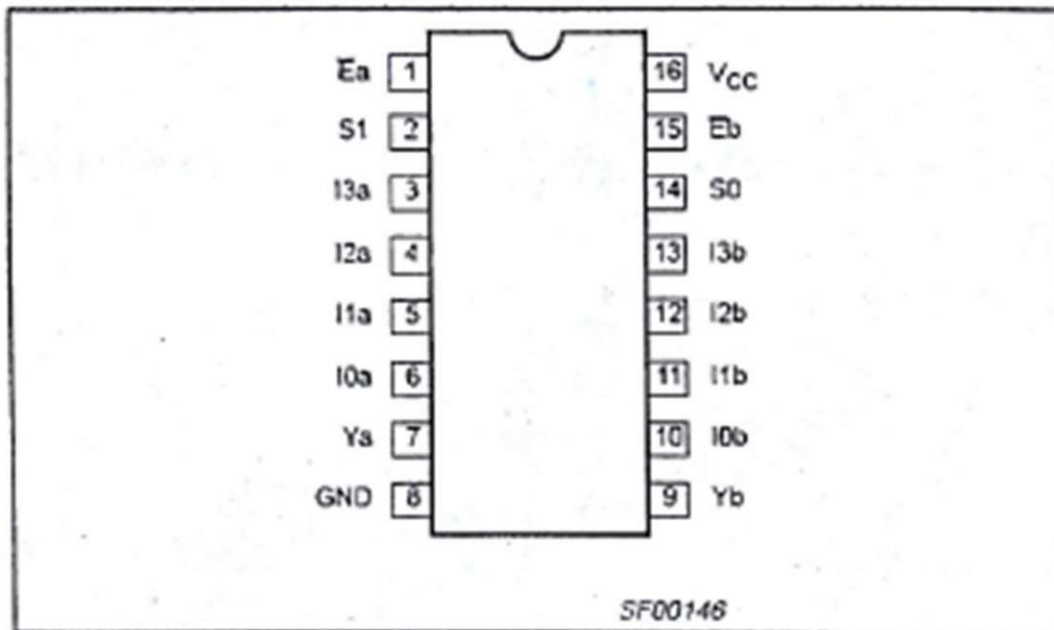

INPUT AND OUTPUT LOADING AND FAN-OUT TABLE

PINS	DESCRIPTION
I0a – I3a	Port A data inputs
I0b – I3b	Port B data inputs
S0, S1	Common Select inputs
Ea	Port A Enable input (active Low)
Eb	Port B Enable input (active Low)
Ya, Yb	Port A, B data outputs