CSE 332 Computer Organizations and Architecture Lab

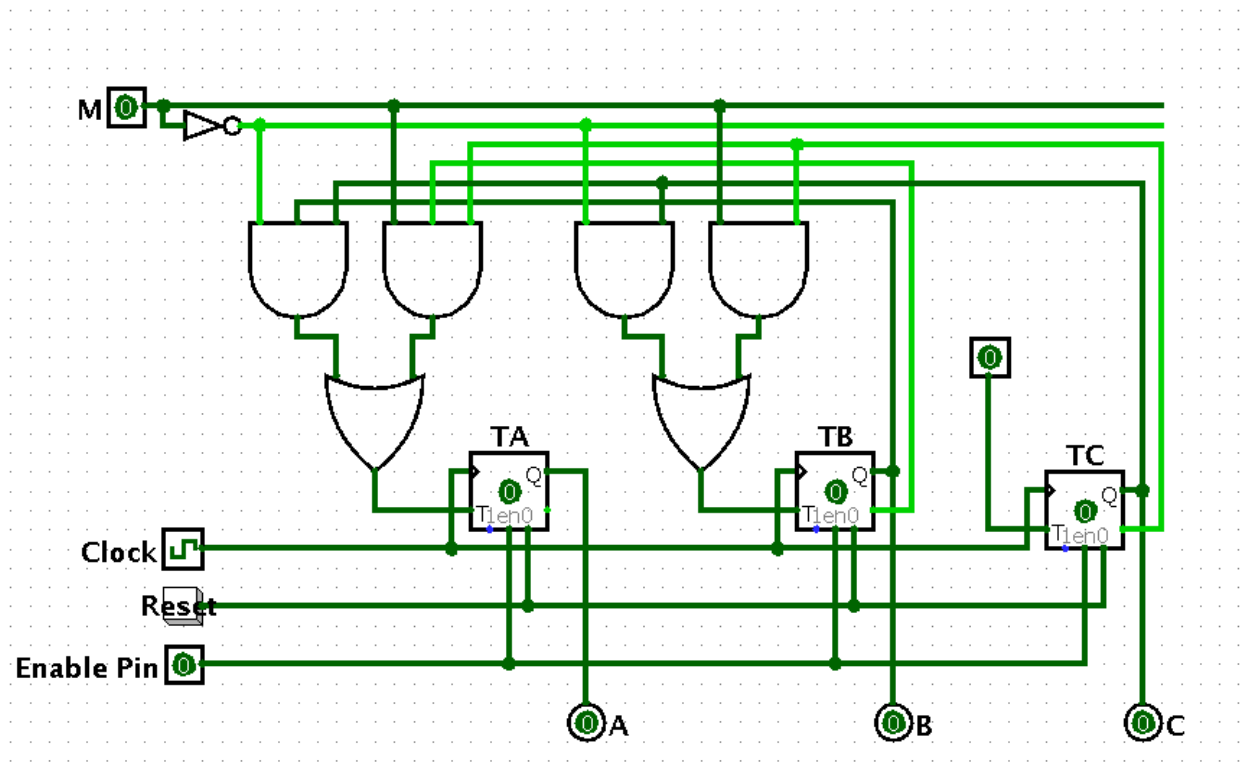**Name: Nazmul Hasan**   **ID: 1911742042**

Logisim: 3 Bit Binary Up-down Counter.

Figure : 3 Bit binary up-down counter.