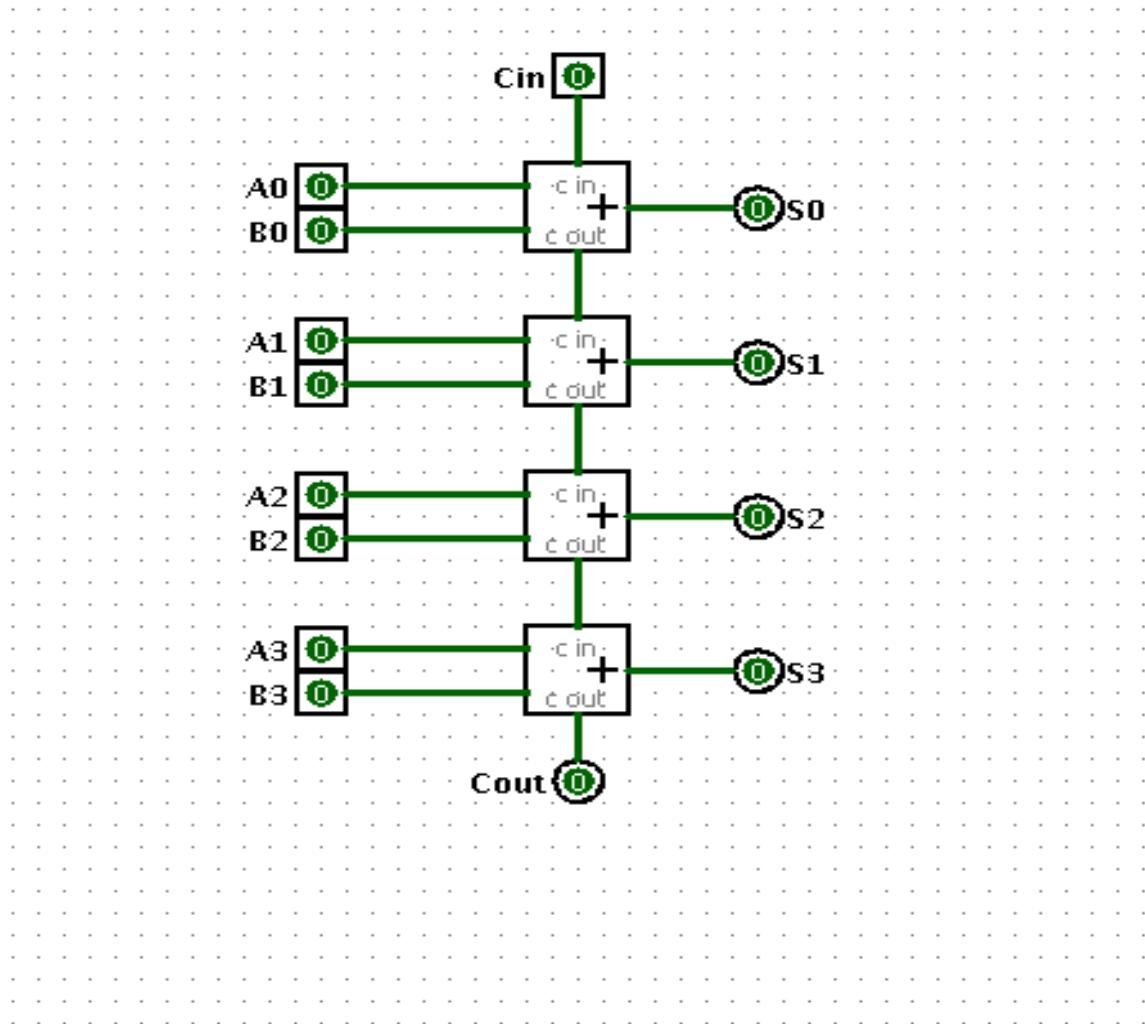**Logisim:** 4-bit Binary Multiplication Unit
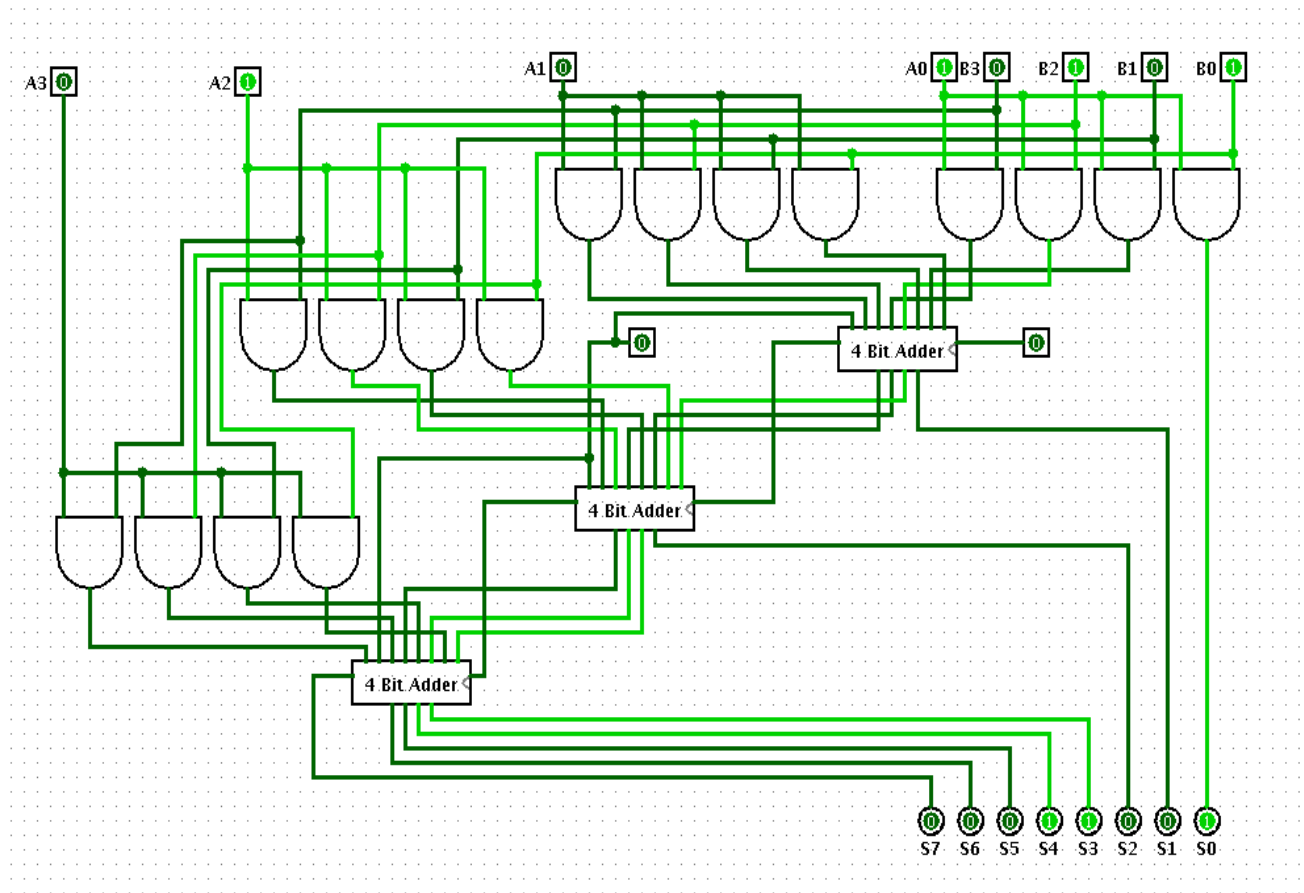

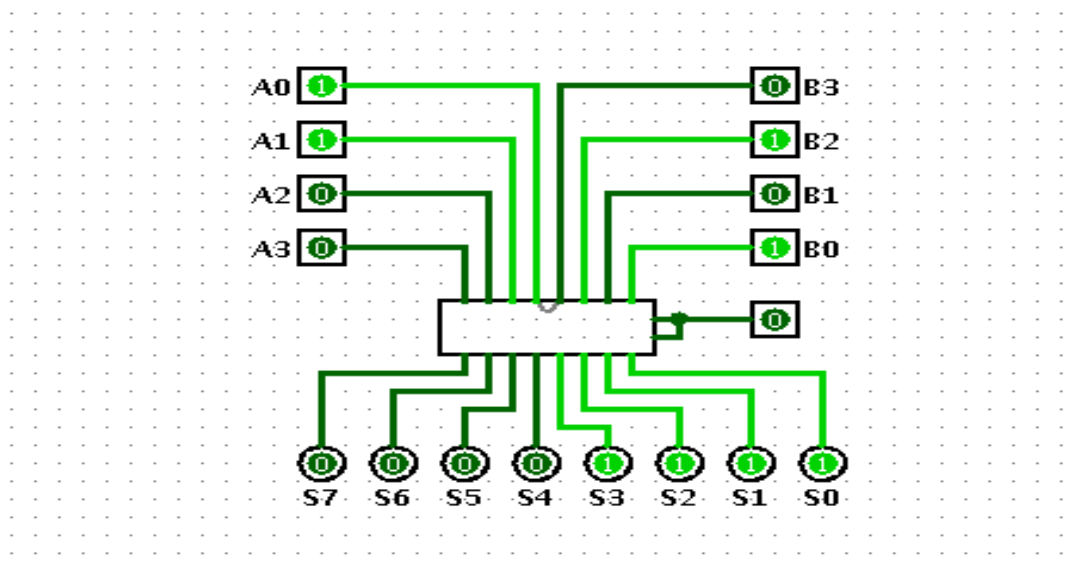Figure: 4 Bit Binary Adder

Figure: 4 Bit Binary Multiplication Unit

Figure: 4 Bit Binary Multiplication Unit (Main Circuit)