CSE 332 Computer Organizations and Architecture Lab

Name: Nazmul Hasan   **ID : 1911742042**

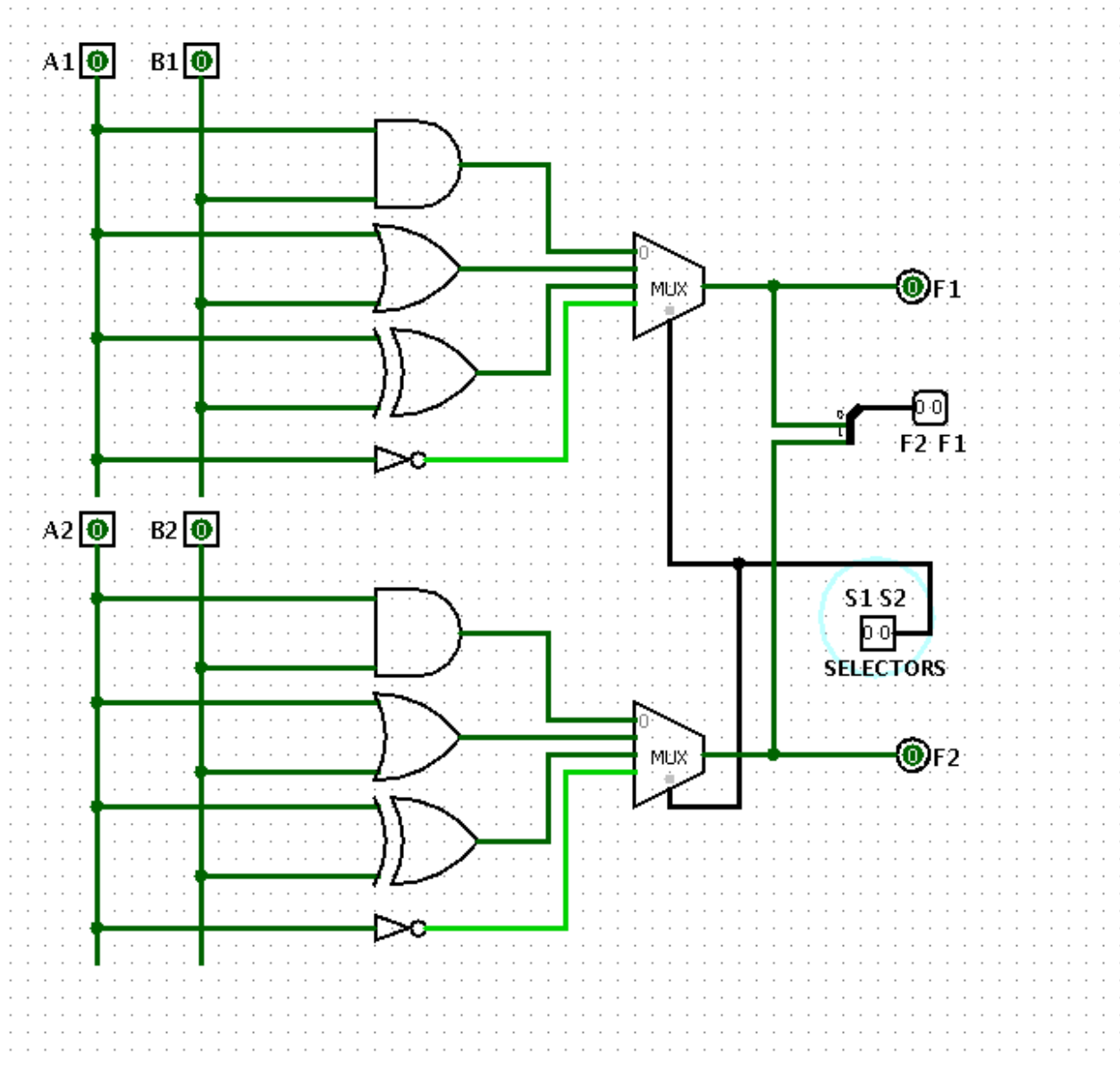**Logisim :** 2 Bit Logic Unit

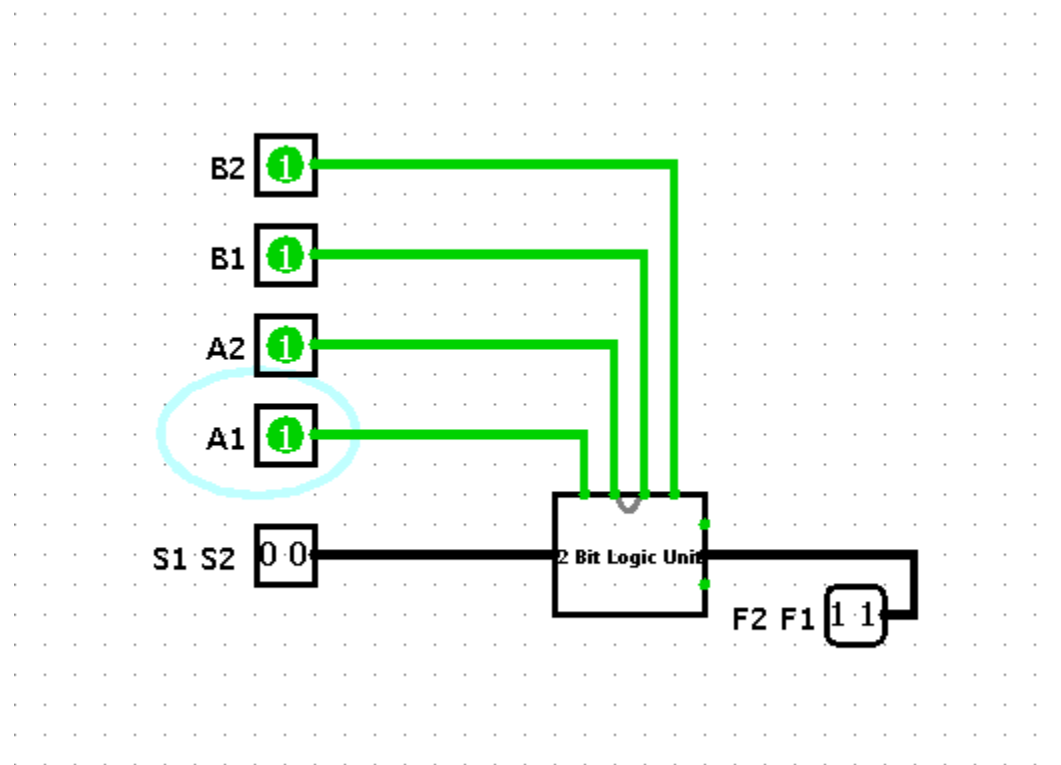

Figure: 2 Bit Logic Unit

Logisim : 2 Bit Logic Unit main circuit

Figure: 2 Bit Logic Unit main circuit